

II B. Tech I Semester Regular Examinations, Jan - 2015**DIGITAL LOGIC DESIGN**

(Com. to CSE, IT)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answer **ALL** the question in **Part-A**
 3. Answer any **THREE** Questions from **Part-B**
- ~~~~~

PART-A

- What are the characteristics of 2's complement numbers?
 - State the purpose of reducing the switching functions to minimal form.
 - Define half adder.
 - What are the basic operations in Boolean algebra?
 - How do you convert one type of flip-flop into another?
 - What are shift registers?
 - What is the basic architecture of a PLA?
 - Compare a decoder with a Demultiplexer. (3M+3M+2M+3M+3M+2M+3M+3M)

PART-B

- The solution to the quadratic equation $x^2 - 11x + 22 = 0$ is $x = 3$ and $x = 6$. What is the base of numbers.
 - Using 10's complement, subtract
 - $72532_{10} - 3250_{10}$
 - $3250_{10} - 72532_{10}$. What do you infer from the results. (8M+8M)
- Using K-map method determine the prime implicant and obtain the possible minimal expression for the following function
 $F(A,B,C,D) = \sum m(8,12,13) + d(1,2,4,6,7,11)$ (16M)
- Implement the following switching function using a Four input multiplexer
 $F(A, B, C, D) = \sum m(0, 1, 2, 4, 6, 9, 10, 13, 14)$
 - A Combinational circuit is defined by the following three Boolean functions
 $F_1 = x'y'z' + xz$ $F_2 = xy'z' + x'y$ $F_3 = x'y'z + xy$
 Design the circuit with a decoder and external gates. (8M+8M)
- Define the following terms related to flip-flops.
 i) set-up time ii) hold time iii) propagation delay iv) preset and v) clear.
 - Discuss D-type edge- triggered flip-flop in detail? (9M+7M)
- Design a resister to perform left shift and right shift for the following data 10110101 ? (16M)
- Implement the following Boolean function using PAL
 i) $F_1(x, y, z) = \sum m(0, 1, 3, 6, 7)$ ii) $F_2(x, y, z) = \sum m(0, 2, 3, 5)$
 - Compare PLA with PROM? (8M+8M)

II B. Tech I Semester Regular Examinations, Jan - 2015**DIGITAL LOGIC DESIGN**

(Com. to CSE, IT)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
2. Answer **ALL** the question in **Part-A**
3. Answer any **THREE** Questions from **Part-B**
- ~~~~~

PART-A

1. a) How are negative numbers represented?
b) What is a cell of a K-map?
c) Define full Subtractor.
d) Write the Boolean algebraic laws.
e) What is meant by race around condition in flip-flops?
f) What is the basic difference between a shift register and a counter?
g) Give the comparison between PROM, PLA, and PAL.
h) What is a standard SOP form? (2M+3M+2M+3M+3M+2M+3M+3M)

PART-B

2. a) What is the advantage of 1's and 2's complement in computers. Represent +45 and -45 in sign-magnitude, sign-1's complement and sign-2's complement representation.
b) Explain about Weighted and non-weighted codes (8M+8M)
3. a) Prove that AND - OR network is equivalent to NAND-NAND network
b) Define the following terms with respect to K-Map with an example.
i) Prime implicant ii) Redundant terms
iii) Essential Prime implicant iv) Octet (8M+8M)
4. a) Implement a full adder with two 4×1 multiplexers.
b) Implement Half adder using 5 NAND gates (8M+8M)
5. a) Convert a T flip flop to D type flip flop.
b) Explain the working of a master-slave JK flip flop. State its advantages. (8M+8M)
6. a) Draw and explain 4-bit universal shift register.
b) Explain different types of shift registers. (8M+8M)
7. List the PLA programming table and draw the PLA structure for the BCD-to-Excess-3-code converter. (16M)

II B. Tech I Semester Regular Examinations, Jan - 2015**DIGITAL LOGIC DESIGN**

(Com. to CSE, IT)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answer **ALL** the question in **Part-A**
 3. Answer any **THREE** Questions from **Part-B**
- ~~~~~

PART-A

1. a) What do you mean by end around carry? When does it come into picture?
- b) What is the importance of Universal Gates?
- c) Define Encoder.
- d) What is a prime implicant in K-map?
- e) Distinguish between synchronous and asynchronous latches?
- f) What are the applications of shift registers?
- g) Is it possible to share the product terms between different outputs in a PLA? If yes, how?
- h) What is the advantage of SOP and POS forms of realization?

(2M+3M+2M+3M+3M+2M+3M+3M)

PART-B

2. a) The binary numbers listed have a sign bit in the left most position and, if negative numbers are in 2's complement form. Perform the arithmetic operations indicated and verify the answers.

i) $101011 + 111000$ ii) $001110 + 110010$ iii) $111001 - 001010$ iv) $101011 - 100110$

- b) Explain about Weighted and non-weighted codes (8M+8M)

3. List out the Basic Theorems and Properties of Boolean Algebra. Justify with Proof. (16M)

4. a) Implement the following functions on decoder logic

 $Y_1 = \Sigma(0,1,3,6,7)$, $Y_2 = \Pi(0,2,4,7)$, $Y_3 = \Pi(1,3,6,7)$

- b) Realize a full sub tractor using MUX. (8M+8M)

5. a) Determine how the circuit shown in Fig. 1 functions as a T-type flip-flop. What problem would there be when $T = 1$ and how could it be resolved.

 


Figure 1

- b) Convert a SR flip-flop to D type flip flop? (8M+8M)
6. a) Draw the logic diagram for a 4-bit binary ripple down counter using positive edge triggered flip-flops.
- b) Explain different types of shift registers. (8M+8M)
7. a) Draw and explain the block diagram of PLA.
- b) Tabulate the PLA programmable table for the four Boolean functions given below:
- $$F_1(x,y,z) = \sum m(1,2,4,6)$$
- $$F_2(x,y,z) = \sum m(0,1,6,7)$$
- $$F_3(x,y,z) = \sum m(2,6)$$
- $$F_4(x,y,z) = \sum m(1,2,3,5,7).$$
- (8M+8M)

II B. Tech I Semester Regular Examinations, Jan - 2015
DIGITAL LOGIC DESIGN
 (Com. to CSE, IT)

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
2. Answer **ALL** the question in **Part-A**
3. Answer any **THREE** Questions from **Part-B**

PART-A

1.
 - a) Why is the binary number system used in digital systems?
 - b) State the Duality principle with example.
 - c) Define Demultiplexer.
 - d) What are the limitations of K-maps?
 - e) What are the various methods used for triggering flip-flops?
 - f) What are the advantages and disadvantages of ripple counters?
 - g) How is the capacity of a PLA specified?
 - h) How do you convert a decimal number into a number in any other system with base b?

PART-B

2. a) Explain how 1's complement and 2's complement of a binary number is obtained? Illustrate by an example.
b) What is gray code? What are the rules to construct gray code? Develop the 4 bit gray code for the decimal 0 to 15. (8M+8M)
3. a) List the universal gates? Implement XOR & XNOR gates using universal gates?
b) Implement the following functions in canonical Sop and Pos forms
i) $f(A, B, C, D) = A'B + BC + CD' + ACD$
ii) $f(A, B, C, D) = (A + B' + C')(A + D)(B' + C')(A + B + C)$ (8M+8M)
4. a) Design an octal to binary encoder.
b) Design a full subtractor and implement it using NAND gates. Explain its operation with the help of truth table? (8M+8M)
5. a) Distinguish between combinational logic and sequential logic.
b) How could:
i) a JK flip-flop be used as a D-type? ii) a JK flip-flop be used as a T-type?
iii) a D-type flip-flop be used as a T-type? (8M+8M)
6. a) Explain synchronous ripple counters. Compare their merits and demerits.
b) Design a modulo -12 up synchronous counter using T- flip flops and draw circuit diagram. (8M+8M)
7. a) Realize the following Boolean function using PROM $f(x, y, z, w) = \sum m(0, 1, 3, 6, 8, 9, 15)$.
b) Implement the following Boolean function using PLA
i) $F_1(x, y, z, w) = \sum m(0, 1, 3, 6, 7), F_2(x, y, z, w) = \sum m(0, 1, 3, 5)$ (8M+8M)