

**II B. Tech I Semester Supplementary Examinations, October/November - 2018****DIGITAL LOGIC DESIGN**

(Com. to CSE, IT)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)2. Answer **ALL** the question in **Part-A**3. Answer any **THREE** Questions from **Part-B****PART -A**

1. a) What is Non weighted code? Write some Non weight codes (4M)
- b) Prove  $AB + \bar{A}C + BC = AB + \bar{A}C$  (3M)
- c) What are advantages of Priority Encoder? (3M)
- d) What is excitation table? write excitation table for JK flip-flop (4M)
- e) Draw the BCD ripple counter logical diagram (4M)
- f) Write the difference between PLA and PROM (4M)

**PART -B**

2. a) Convert the decimal numbers 350.5, 14.0625,  $10^2$ , 673.23 to binary, base 4, base 6, base 8, base 16. (8M)
- b) Is it possible to construct a 5 4 1 1 weighted code and also a 6 3 2 1 Weighted code? Justify your answer (8M)
3. a) Express the following function as a sum of min terms and as a product of max terms:  $F(A, B, C, D) = \bar{B}D + \bar{A}D + BD$  (8M)
- b) Simplify the following Boolean function  $F(A, B, C, D) = \pi(1, 3, 5, 7, 13, 15)$  (8M)
4. a) Explain about Ripple Adder/Subtractor using 1's complement method (8M)
- b) Implement a full adder with two 4 X1 multiplexers (8M)
5. a) What is a master slave flip flop? Design a clocked master slave JK flip flop (8M)
- b) Conversion of JK flip flop to D flip flop (8M)
6. a) Draw the logic diagram of a 4 bit register with four D flip-flop and four 4X1 MUXs with mode selection inputs  $s_1$  and  $s_0$ . The register operates according to the following function table: (8M)

$S_1$	$S_0$	Register operation
0	0	No change
0	1	Complement the four outputs
1	0	Clear register to 0
1	1	Load parallel data

- b) Design a 4-bit binary synchronous counter with D flip-flop (8M)
7. A Combinational circuit defined by functions (16M)
 
$$A(x, y, z) = \sum (1, 2, 4, 6) \quad B(x, y, z) = \sum (0, 1, 6, 7)$$

$$C(x, y, z) = \sum (2, 6) \quad D(x, y, z) = \sum (1, 2, 3, 5, 7)$$

Implement circuit with 8X4 ROM

WWW.MANARESULTS.CO.IN