


## Bidirectional Counters

Bidirectional counters are capable of counting in either the up direction or the down direction through any given count sequence

As well as counting “up” from zero and increasing or incrementing to some preset value, it is sometimes necessary to count “down” from a predetermined value to zero allowing us to produce an output that activates when the zero count or some other pre-set value is reached.

This type of counter is normally referred to as a **Down Counter**, (CTD). In a binary or BCD down counter, the count decreases by one for each external clock pulse from some preset value. Special dual purpose IC's such as the TTL 74LS193 or CMOS CD4510 are 4-bit binary Up or Down counters which have an additional input pin to select either the up or down count mode.

### 4-bit Count Down Counter

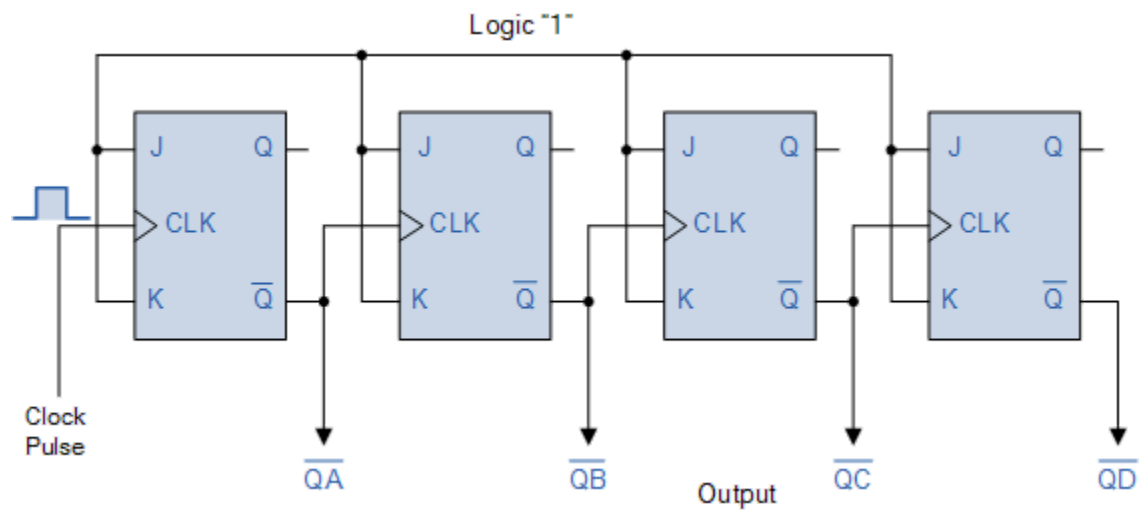



In the 4-bit counter above the output of each flip-flop changes state on the falling edge (1-to-0 transition) of the CLK input which is triggered by the  $\overline{Q}$  output of the previous flip-flop, rather than by the Q output as in the up counter configuration. As a result, each flip-flop will change state when the previous one changes from 0 to 1 at its output, instead of changing from 1 to 0.

## Bidirectional Counter

Both Synchronous and Asynchronous counters are capable of counting “Up” or counting “Down”, but there is another more “Universal” type of counter that can count in both directions either Up or Down depending on the state of their input control pin and these are known as **Bidirectional Counters**.

*Bidirectional counters*, also known as Up/Down counters, are capable of counting in either direction through any given count sequence and they can be reversed at any point within their count sequence by using an additional control input as shown below.

## Synchronous 3-bit Up/Down Counter

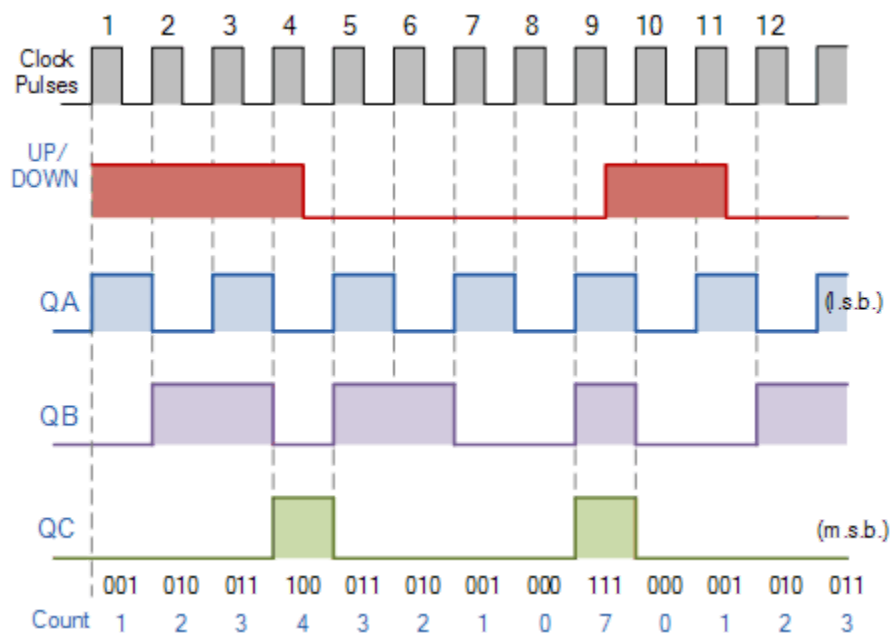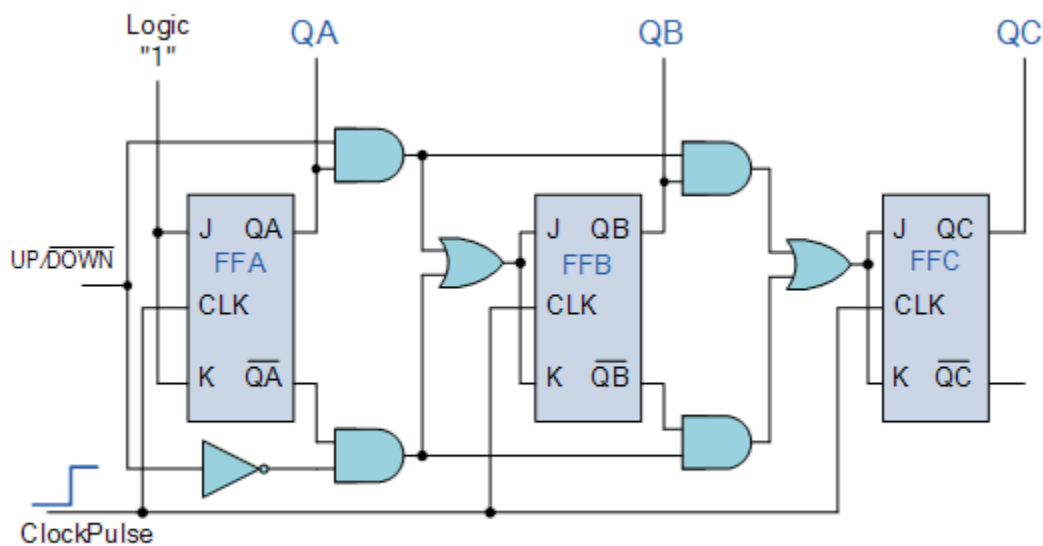

The circuit above is of a simple 3-bit Up/Down synchronous counter using JK flip-flops configured to operate as toggle or T-type flip-flops giving a maximum count of zero (000) to seven (111) and back to zero again. Then the 3-Bit counter advances upward in sequence (0,1,2,3,4,5,6,7) or downwards in reverse sequence (7,6,5,4,3,2,1,0).

Generally most bidirectional counter chips can be made to change their count direction either up or down at any point within their counting sequence. This is achieved by using an additional input pin which determines the direction of the count, either Up or Down and the timing diagram gives an example of the counters operation as this Up/Down input changes state.

Nowadays, both up and down counters are incorporated into single IC that is fully programmable to count in both an "Up" and a "Down" direction from any preset value producing a complete **Bidirectional Counter** chip. Common chips available are the 74HC190 4-bit BCD decade Up/Down counter, the 74F569 is a fully synchronous Up/Down binary counter and the CMOS 4029 4-bit Synchronous Up/Down counter.

# 52 Comments

---

Join the conversation

Your Name

Email Address

Write your comment here

SUBMIT

J Jainam Mehta

Nice presentation

Posted on November 16th 2018 | 2:03 pm

← Reply



Dom

Also, thanks. This is super useful

Posted on November 11th 2018 | 6:47 pm

← Reply



Dom

I'm pretty sure there's an error at the end of the timing diagram. It should end with 1 0 7, not 1 2 3.

Posted on November 11th 2018 | 6:47 pm

← Reply



Dom

"In the 4-bit counter above the output of each flip-flop changes state on the falling edge (1-to-0 transition) of the CLK input which is triggered by the Q output of the previous flip-flop, rather than by the Q output as in the up counter configuration."

Doesn't the value of Q and !Q remain the same when the CLK falls?

Posted on November 11th 2018 | 6:08 pm

← Reply

---

L Lavkush

Very good sir

Posted on October 11th 2018 | 3:12 am

← Reply

---

s saqlain khaan

nice

Posted on September 27th 2018 | 2:41 pm

← Reply

---

**d** dan diaz

trying to get a 20 position roundhouse turntable to stop at a programmed position

Posted on June 05th 2018 | 1:28 pm

 Reply

---

**R** Ranjana mourya

Not satisfied of this explanation of 3 bit up down syn .C.

Posted on April 03rd 2018 | 5:15 am

 Reply

---

**D** Delowar Hossen

I want to doing better performance in Electronics.So,I should join this group

Posted on March 31st 2018 | 12:13 pm

 Reply

---

**S** Shalu kandari

I like this

Posted on March 26th 2018 | 4:52 pm

 Reply

---

[View More](#)