

## The JK Flip Flop

The JK Flip-flop is similar to the SR Flip-flop but there is no change in state when the J and K inputs are both LOW

The basic S-R NAND flip-flop circuit has many advantages and uses in sequential logic circuits but it suffers from two basic switching problems.

1. the Set = 0 and Reset = 0 condition ( $S = R = 0$ ) must always be avoided
2. if Set or Reset change state while the enable (EN) input is high the correct latching action may not occur


Then to overcome these two fundamental design problems with the SR flip-flop design, the **JK flip Flop** was developed.

This simple **JK flip Flop** is the most widely used of all the flip-flop designs and is considered to be a universal flip-flop circuit. The two inputs labelled "J" and "K" are not shortened abbreviated letters of other words, such as "S" for Set and "R" for Reset, but are themselves autonomous letters chosen by its inventor Jack Kirby to distinguish the flip-flop design from other types.

The sequential operation of the JK flip flop is exactly the same as for the previous SR flip-flop with the same “Set” and “Reset” inputs. The difference this time is that the “JK flip flop” has no invalid or forbidden input states of the SR Latch even when S and R are both at logic “1”.

The **JK flip flop** is basically a gated SR flip-flop with the addition of a clock input circuitry that prevents the illegal or invalid output condition that can occur when both inputs S and R are equal to logic level “1”. Due to this additional clocked input, a JK flip-flop has four possible input combinations, “logic 1”, “logic 0”, “no change” and “toggle”. The symbol for a JK flip flop is similar to that of an *SR Bistable Latch* as seen in the previous tutorial except for the addition of a clock input.

## The Basic JK Flip-flop

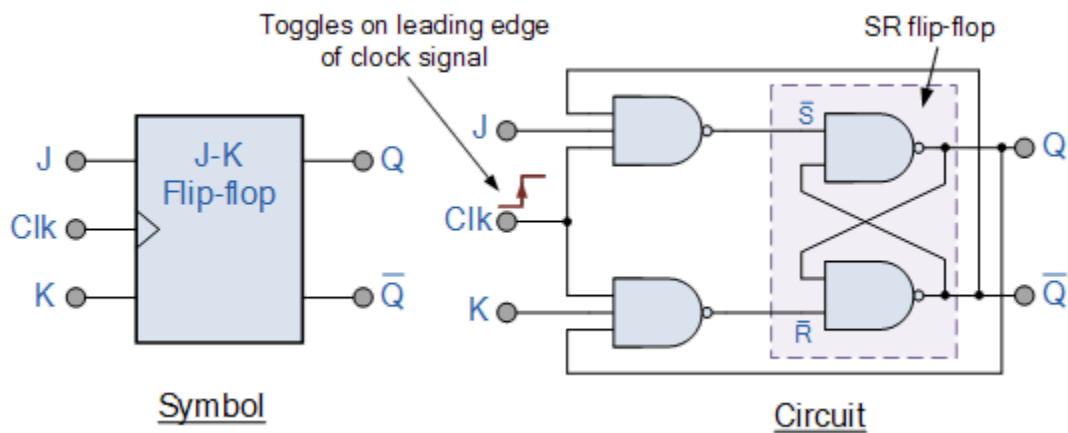

Both the S and the R inputs of the previous SR bistable have now been replaced by two inputs called the J and K inputs, respectively after its inventor Jack Kilby. Then this equates to:  $J = S$  and  $K = R$ .

The two 2-input AND gates of the gated SR bistable have now been replaced by two 3-input NAND gates with the third input of each gate connected to the outputs at Q and  $\bar{Q}$ . This cross coupling of the SR flip-flop allows the previously invalid condition of  $S = "1"$  and  $R = "1"$  state to be used to produce a “toggle action” as the two inputs are now interlocked.

If the circuit is now “SET” the J input is inhibited by the “0” status of  $\bar{Q}$  through the lower NAND gate. If the circuit is “RESET” the K input is inhibited by the “0” status of Q through the upper NAND gate. As Q and  $\bar{Q}$  are always different we can use them to control the input. When both inputs J and K are equal to logic “1”, the JK flip flop toggles as shown in the following truth table.

## The Truth Table for the JK Function

| same as<br>for the<br>SR Latch | Input |   | Output |           | Description |
|--------------------------------|-------|---|--------|-----------|-------------|
|                                | J     | K | Q      | $\bar{Q}$ |             |
|                                |       |   |        |           |             |

|                  |   |   |   |   |                     |
|------------------|---|---|---|---|---------------------|
| toggle<br>action | 0 | 0 | 0 | 0 | Memory<br>no change |
|                  | 0 | 0 | 0 | 1 |                     |
|                  | 0 | 1 | 1 | 0 | Reset Q » 0         |
|                  | 0 | 1 | 0 | 1 |                     |
|                  | 1 | 0 | 0 | 1 | Set Q » 1           |
|                  | 1 | 0 | 1 | 0 |                     |
|                  | 1 | 1 | 0 | 1 | Toggle              |
|                  | 1 | 1 | 1 | 0 |                     |

Then the JK flip-flop is basically an SR flip flop with feedback which enables only one of its two input terminals, either SET or RESET to be active at any one time thereby eliminating the invalid condition seen previously in the SR flip flop circuit.

Also when both the J and the K inputs are at logic level “1” at the same time, and the clock input is pulsed “HIGH”, the circuit will “toggle” from its SET state to a RESET state, or visa-versa. This results in the JK flip flop acting more like a T-type toggle flip-flop when both terminals are “HIGH”.


Although this circuit is an improvement on the clocked SR flip-flop it still suffers from timing problems called “race” if the output Q changes state before the timing pulse of the clock input has time to go “OFF”. To avoid this the timing pulse period ( T ) must be kept as short as possible (high frequency). As this is sometimes not possible with modern TTL IC’s the much improved **Master-Slave JK Flip-flop** was developed.

## Master-Slave JK Flip-flop

The master-slave flip-flop eliminates all the timing problems by using two SR flip-flops connected together in a series configuration. One flip-flop acts as the “Master” circuit, which triggers on the leading edge of the clock pulse while the other acts as the “Slave” circuit, which triggers on the falling edge of the clock pulse. This results in the two sections, the master section and the slave section being enabled during opposite half-cycles of the clock signal.

The TTL 74LS73 is a Dual JK flip-flop IC, which contains two individual JK type bistable’s within a single chip enabling single or master-slave toggle flip-flops to be made. Other JK flip flop IC’s include the 74LS107 Dual JK flip-flop with clear, the 74LS109 Dual positive-edge triggered JK flip flop and the 74LS112 Dual negative-edge triggered flip-flop with both preset and clear inputs.

## Dual JK Flip-flop 74LS73

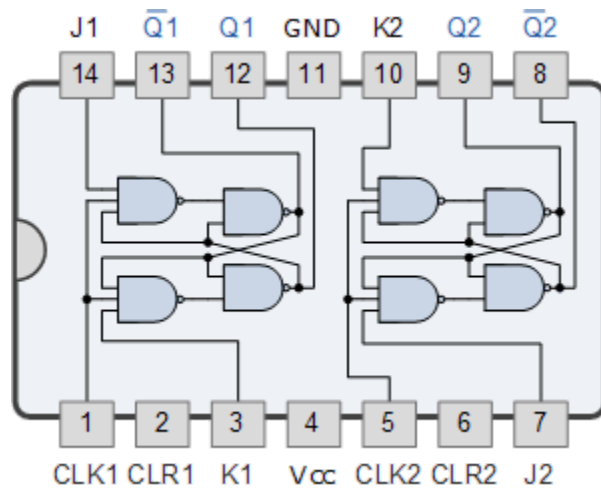


### Other Popular JK Flip-flop ICs

| Device Number | Subfamily     | Device Description                            |
|---------------|---------------|---|
| 74LS73        | LS TTL        | Dual JK-type Flip Flops with Clear            |
| 74LS76        | LS TTL        | Dual JK-type Flip Flops with Preset and Clear |
| 74LS107       | LS TTL        | Dual JK-type Flip Flops with Clear            |
| 4027B         | Standard CMOS | Dual JK-type Flip Flop                        |

### The Master-Slave JK Flip-flop

The **Master-Slave Flip-Flop** is basically two gated SR flip-flops connected together in a series configuration with the slave having an inverted clock pulse. The outputs from Q and  $\overline{Q}$  from the “Slave” flip-flop are fed back to the inputs of the “Master” with the outputs of the “Master” flip flop being connected to the two inputs of the “Slave” flip flop. This feedback configuration from the slave’s output to the master’s input gives the characteristic toggle of the JK flip flop as shown below.

### The Master-Slave JK Flip Flop

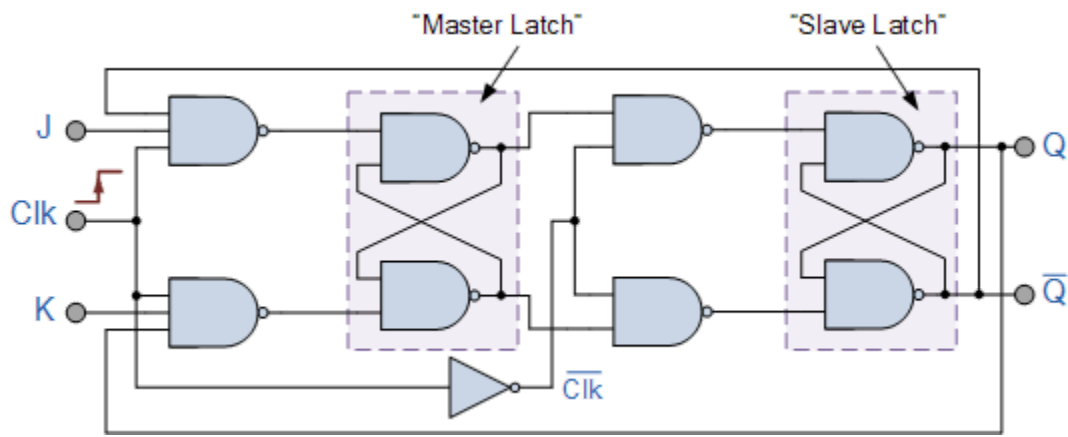

The input signals J and K are connected to the gated “master” SR flip flop which “locks” the input condition while the clock (Clk) input is “HIGH” at logic level “1”. As the clock input of the “slave” flip flop is the inverse (complement) of the “master” clock input, the “slave” SR flip flop does not toggle. The outputs from the “master” flip flop are only “seen” by the gated “slave” flip flop when the clock input goes “LOW” to logic level “0”.

When the clock is “LOW”, the outputs from the “master” flip flop are latched and any additional changes to its inputs are ignored. The gated “slave” flip flop now responds to the state of its inputs passed over by the “master” section.

Then on the “Low-to-High” transition of the clock pulse the inputs of the “master” flip flop are fed through to the gated inputs of the “slave” flip flop and on the “High-to-Low” transition the same inputs are reflected on the output of the “slave” making this type of flip flop edge or pulse-triggered.

Then, the circuit accepts input data when the clock signal is “HIGH”, and passes the data to the output on the falling-edge of the clock signal. In other words, the **Master-Slave JK Flip flop** is a “Synchronous” device as it only passes data with the timing of the clock signal.

In the next tutorial about **Sequential Logic Circuits**, we will look at *Multivibrators* that are used as waveform generators to produce the clock signals to switch sequential circuits.

## 135 Comments

---

Join the conversation

Your Name

Email Address

Write your comment here

SUBMIT

I Ishu

Thanks

Posted on October 23rd 2018 | 3:23 pm

← Reply

J Javed

Welcome.. ishu

Posted on October 23rd 2018 | 6:37 pm

← Reply

---

A Anik mahmud

it is batter of characteristic table and excitation table in given this tutorials.....

Posted on October 10th 2018 | 4:16 am

← Reply

---

**B** BASHIR SHUAIBU Ahmad

what do u understand by jk

Posted on October 09th 2018 | 1:28 pm

← Reply

---

**S** Shripad Govekar

Excellent.....

Posted on October 08th 2018 | 5:55 pm

← Reply

---

**M** M.Mohamed Rizwan

what does j and k stands for?

Posted on October 08th 2018 | 1:13 pm

← Reply



Shubham Upadhyay

They are inputs, they can be high or low or 1 or zero  
J-k stands for Jack Kilby.

Posted on October 08th 2018 | 4:13 pm

← Reply

---

**P** Prakash Saini

Thanks

Posted on October 05th 2018 | 3:38 pm

← Reply

---

T Tejas Naik

L

Posted on September 30th 2018 | 6:42 pm

← Reply

---

S Saisree Komma

What are  $q_n$  and  $q_{n+1}$

Posted on September 19th 2018 | 2:21 am

← Reply

---

B BASANTA KUMAR PARIDA

i learnt new thing.

Posted on September 14th 2018 | 4:12 am

← Reply

---

N Nitesh Nagwani

what is the ans? for this then

Posted on June 29th 2018 | 8:42 am

← Reply

---

View More